

RC Circuit

Lab #3

Name: Aidan Fitzgerald
Partner: Jared Beh

June 7, 2016

RC Circuit

Objective

Infer the relationship between the time constant τ , resistance R , and capacitance C of an RC circuit.

1 Introduction

An RC circuit is a type of circuit made of a resistor and a capacitor connected in series, like so:

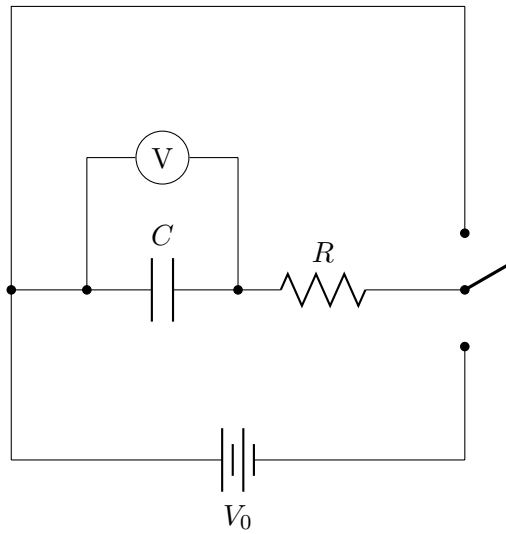


Figure 1: RC circuit

When a constant DC voltage V_0 is applied to the circuit, an electric field builds up inside the capacitor as it gradually charges. By Kirchhoff's voltage law, the circuit's behavior as a function of time is given by the first-order differential equation

$$V_0 - \frac{Q}{C} - R\dot{Q} = 0 \quad (1)$$

The solution to this equation is

$$V(t) = V_0 (1 - e^{-t/RC}) \quad (2)$$

As t approaches infinity, $V(t)$ approaches V_0 .

The time constant τ of an RC circuit is defined such that

$$V(\tau) = V_0 (1 - e^{-1}) \approx 0.63 V_0. \quad (3)$$

Therefore,

$$\tau = RC. \quad (4)$$

Note that τ does not depend on V_0 : the greater the applied voltage, the faster the capacitor charges.

When a capacitor is discharging into an RC circuit, it produces an exponentially decaying direct current. As a function of time, this is

$$V(t) = V_0 e^{-t/\tau} \quad (5)$$

Substituting $t = \tau$,

$$V(\tau) = V_0 e^{-1} \approx 0.37 V_0. \quad (6)$$

2 Procedures and Results

We set up the circuit shown in Figure 1. We set V_0 to 4.5 V, R to 1.6 k Ω , and C to 27 mF. We turned on the power and took voltage measurements every 5 seconds for 45 seconds.

Table 1: Charging from a 4.5-V DC power source.

Time (s)	Voltage (V)	% of V_0
0	0	0.00%
5	1.01	22.44%
10	2.04	45.33%
15	2.93	65.11%
20	3.27	72.67%
25	3.31	73.56%
30	3.26	72.44%
35	3.22	71.56%
40	3.2	71.11%
45	3.18	70.67%

Next, we turned off the power and quickly disconnected the DC power source, so that the capacitor began to discharge. We took voltage measurements every 5 seconds for 60 seconds.

Table 2: Discharging after a 45-s charge.

Time (s)	Voltage (V)	% of V_0
0	3.18	100.00%
5	2.39	75.16%
10	2.11	66.35%
15	1.88	59.12%
20	1.69	53.14%
25	1.53	48.11%
30	1.38	43.40%
35	1.24	38.99%
40	1.12	35.22%
45	1.02	32.08%
50	0.92	28.93%
55	0.84	26.42%
60	0.72	22.64%

Then, we repeated these steps with a $200\ \Omega$ resistor and $V_0 = 12\ \text{V}$.

Table 3: Charging with a $200\ \Omega$ resistor for 60 s.

Time (s)	Voltage (V)	% of V_0
0	0	0.00%
5	6.14	51.17%
10	8.92	74.33%
15	10.33	86.08%
20	10.98	91.50%
25	11.34	94.50%
30	11.53	96.08%
35	11.62	96.83%
40	11.67	97.25%
45	11.71	97.58%
50	11.73	97.75%
55	11.74	97.83%
60	11.75	97.92%

Table 4: Discharging for 70 s.

Time (s)	Voltage (V)	% of V_0
0	11.76	100.00%
5	5.05	42.94%
10	2.36	20.07%
15	1.24	10.54%
20	0.67	5.70%
25	0.35	2.98%
30	0.2	1.70%
35	0.13	1.11%
40	0.08	0.68%
45	0.06	0.51%
50	0.04	0.34%
55	0.03	0.26%
60	0.02	0.17%
65	0.02	0.17%
70	0.02	0.17%

3 Discussion

We know from Eq. 3 that during charging, the voltage rises to about 63% of its maximum level after one time constant. In Table 1, this occurs at roughly 15 s. This implies that $\tau \approx 15$ s. Using Eq. 4, we obtained an accepted value of $\tau = RC = (1600\ \Omega)(27\ \text{mF}) = 43.2$ s. The percent error was 65%.

Similarly, by Eq. 6, during discharging, the voltage drops to about 37% of its original level after one time constant. In Table 2, this occurs between 10 s and 15 s, yielding $\tau \approx 12.5$ s. Again, the accepted value of τ is 43.2 s. The percent error was 71%.

In Table 3, the time constant observed during charging was between 5 s and 10 s, or approximately 7.5 s. In Table 4, the time constant observed during discharging was between 5 s and 10 s as well. The accepted value was $\tau = RC = (200\ \Omega)(27\ \text{mF}) = 5.4$ s. The percent error was 39%.

4 Conclusion

The voltage in an RC circuit decays at a rate proportional to the product of the resistance and the capacitance, called the time constant, τ .