

# RC Circuit with Oscilloscope

Lab #5

Name: Aidan Fitzgerald

Partners: Jason Shin, Victor Tan, and ???

June 7, 2016

## RC Circuit with Oscilloscope

### Objective

Use an oscilloscope to observe the time constant of an RC circuit experimentally.

### 1 Introduction

Recall from Lab #3 that the time constant  $\tau$  of an RC circuit is the time during which the voltage decays to  $1/e \approx 37\%$  of its value. The time constant is equal to  $RC$ .

An analog oscilloscope is an electronic device that plots voltage as a function of time by deflecting an electron beam in a cathode ray tube. In our setup it takes the place of a voltmeter.

### 2 Procedures and Results

We set up the circuit according to Figure 1, using an oscilloscope as a voltmeter and a function generator in place of a battery.


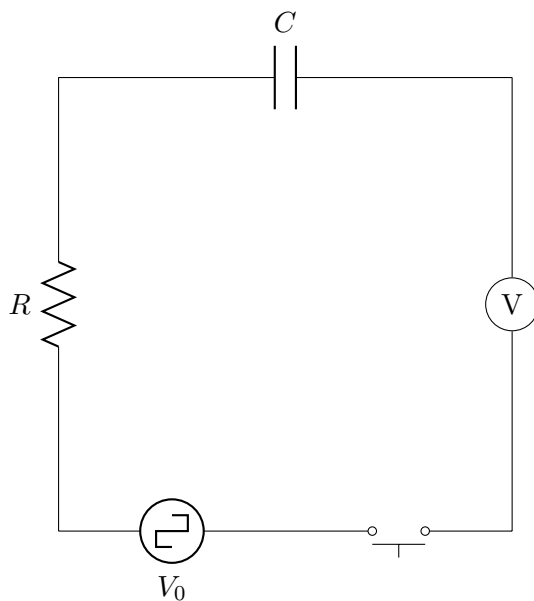



Figure 1: RC circuit

We set the function generator to produce a square wave and observed an output signal that looked like a series of spikes:

### Differentiator

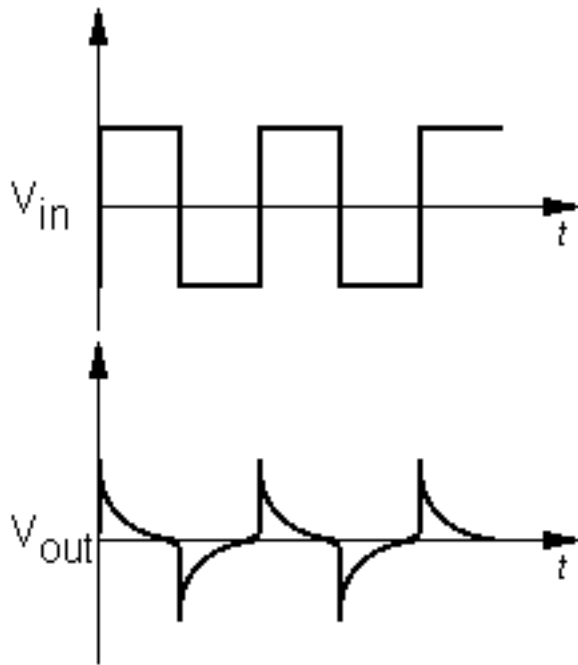

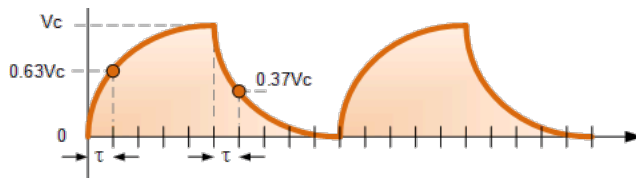We then set the function generator to produce a triangle wave and observed an output signal that looked more like this:



which is more like the waveform we were told would appear. We adjusted the SEC/DIV knob of the oscilloscope until the image was frozen on the screen and adjusted VOLTS/DIV so that the waveform was 8 boxes high. Then, we measured the number of boxes across which the signal rose by 5 boxes.

Table 1: Oscilloscope measurements. Data courtesy of Margaret Burkart

Trial	Resistance	Capacitance	Divisions across	SEC/DIV
1	10,920 $\Omega$	900 pF	1.2	20 $\mu s$
2	5,555 $\Omega$	900 pF	1.9	20 $\mu s$
3	1,111 $\Omega$	900 pF	1.9	20 $\mu s$
4	5,555 $\Omega$	100 pF	1.8	20 $\mu s$
5	5,555 $\Omega$	500 pF	1.9	20 $\mu s$

### 3 Discussion

We calculated the observed time constant by multiplying the divisions across by the value of the SEC/DIV knob. A sample calculation is shown for Trial 1:

$$\tau_{observed} = 1.2 \times 20 \mu s = 24 \mu s$$

We calculated an accepted value for  $\tau$  by multiplying the resistance by the capacitance:

$$\tau_{accepted} = 10,920 \Omega \times 900 \text{ pF} = 9.828 \mu s$$

Then, we calculated the percent error:

$$\% \text{ error} = \frac{|\tau_{observed} - \tau_{accepted}|}{\tau_{accepted}} = \frac{|24 \mu s - 9.828 \mu s|}{9.828 \mu s} = 144\%$$

Table 2: Oscilloscope measurements. Data courtesy of Margaret Burkart

Trial	$\tau_{observed}$	$\tau_{accepted}$	% error
1	24 $\mu s$	9.828 $\mu s$	144 %
2	38 $\mu s$	4.9995 $\mu s$	660 %
3	38 $\mu s$	999.9 ns	3700%
4	36 $\mu s$	555.5 ns	6381%
5	38 $\mu s$	2.7775 $\mu s$	1268%

### 4 Conclusion

Today