

RC Circuit

Lab #3

Name: Aidan Fitzgerald
Partner: Jared Beh

June 7, 2016

RC Circuit

Objective

Infer the relationship between the time constant τ , resistance R , and capacitance C of an RC circuit.

1 Introduction

An RC circuit is a type of circuit made of a resistor and a capacitor connected in series, like so:

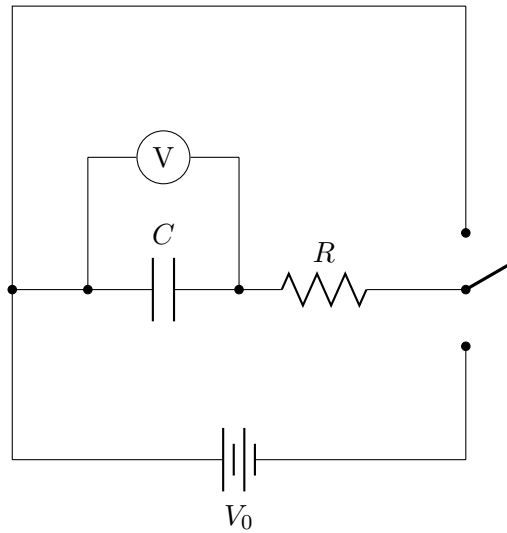


Figure 1: RC circuit

When a constant DC voltage V_0 is applied to the circuit, an electric field builds up inside the capacitor as it gradually charges. By Kirchhoff's voltage law, the circuit's behavior as a function of time is given by the first-order differential equation

$$V_0 - \frac{Q}{C} - R\dot{Q} = 0 \quad (1)$$

The solution to this equation is

$$V(t) = V_0 (1 - e^{-t/RC}) \quad (2)$$

As t approaches infinity, $V(t)$ approaches V_0 .

The time constant τ of an RC circuit is defined such that

$$V(\tau) = V_0 (1 - e^{-1}) \approx 0.63 V_0. \quad (3)$$

Therefore,

$$\tau = RC. \quad (4)$$

Note that τ does not depend on V_0 : the greater the applied voltage, the faster the capacitor charges.

When a capacitor is discharging into an RC circuit, it produces an exponentially decaying direct current. As a function of time, this is

$$V(t) = V_0 e^{-t/\tau} \quad (5)$$

We can graph the logarithm of voltage as a linear function of time. From Eq. 2, we obtain

$$\ln(V_0 - V) = -\frac{t}{RC} + \ln V_0 \quad (6)$$

and from Eq. 5, we get

$$\ln V = -\frac{t}{RC} + \ln V_0 \quad (7)$$

2 Procedures and Results

We set up the circuit shown in Figure 1.

3 Discussion

You

4 Conclusion

Today